

Deductive Fault Simulator Report

- Jackson Miller
- 11/8/2024
- ECE 6140

The deductive fault simulator builds off of the previous fault-free simulation technique. I improved and organized the program architecture, and made use of automated unit testing.

Here is an example of using the FaultSimulator class, taken from scripts/coverage.

```
from simulator import FaultSimulator

netlist = 'circuits/s27.net'
vector = '1110101'
sim = FaultSimulation(netlist)
faults = sim.detect_faults(vector)

print(faults)
```

The deductive fault simulator propagates a fault list L to output Z according to the equations below. C is the set of gate inputs at the controlling value c .

$$\begin{aligned} \text{if } C = \emptyset \text{ then } L_Z &= \left\{ \bigcup_{j \in I} L_j \right\} \cup \{Z \text{ s-a-}(c \oplus i)\} \\ \text{else } L_Z &= \left\{ \bigcap_{j \in C} L_j \right\} - \left\{ \bigcup_{j \in I-C} L_j \right\} \cup \{Z \text{ s-a-}(\bar{c} \oplus i)\} \end{aligned}$$

Part (a)

Below is a summary of the results of detecting faults on the various given circuits. See Appendix B for the entire list of faults detected by each test vector.

Table 1: Fault simulation summary

File	Test	# Detected Faults
s27	1101101	9
s27	0101001	13
s298f_2	101010111110010101	87
s298f_2	11101110101110111	53
s344f_2	10101010101011110111111	82
s344f_2	111010111010101010001100	132
s349f_2	10100000001010101111111	97
s349f_2	111111101010101010001111	137

Part (b)

Each netlist was simulated with random vectors to calculate fault coverage

$$\text{coverage} = \frac{\text{found_faults}}{N} * 100\%$$

where N is the total number of possible stuck-at faults in the circuit, $2 * \text{total_nets}$.

The table summarizes the findings over an average of 15 sets of random test vectors. Because of the nature of random vectors, every trial is different.

Table 2: Coverage test summary

File	Total # Faults	Tests for 75% coverage	Tests for 90% coverage
s27.net	20	7.9	17.7
s298f_2.net	202	18.1	49.5
s344f_2.net	190	9.1	22.9
s349f_2.net	189	9.4	21.8

 


Figure 1: Plot of coverage for each circuit.

Appendix A

User Manual: Fault Simulator and PODEM

Appendix B

Circuit: s27

- Input Vector: 1 1 0 1 1 0 1
- Detected Faults: 9

Table 3: s27 (1101101)

1 s-a-0	3 s-a-1	5 s-a-0	7 s-a-0	9 s-a-1	11 s-a-0	12 s-a-0	13 s-a-0	15 s-a-1
---------	---------	---------	---------	---------	----------	----------	----------	----------

Circuit: s27

- Input Vector: 0 1 0 1 0 0 1
- Detected Faults: 13

Table 4: s27 (0101001)

1 s-a-1	3 s-a-1	5 s-a-0	7 s-a-1	8 s-a-1	9 s-a-1	11 s-a-0	12 s-a-1	14 s-a-0
15 s-a-1	16 s-a-1	19 s-a-1	20 s-a-1					

Circuit: s298f_2

- Input Vector: 1 0 1 0 1 0 1 1 1 1 0 0 1 0 1 0 1
- Detected Faults: 87

Table 5: s298f_2 (10101011110010101)

3 s-a-0	5 s-a-0	6 s-a-1	7 s-a-0	8 s-a-0	9 s-a-0	10 s-a-0	11 s-a-1
12 s-a-1	15 s-a-0	18 s-a-1	19 s-a-1	20 s-a-1	21 s-a-1	22 s-a-1	23 s-a-1
24 s-a-0	25 s-a-0	26 s-a-0	27 s-a-0	28 s-a-1	29 s-a-1	30 s-a-1	31 s-a-1
32 s-a-0	33 s-a-1	34 s-a-0	35 s-a-0	36 s-a-1	37 s-a-0	39 s-a-1	41 s-a-1
45 s-a-1	48 s-a-0	49 s-a-0	50 s-a-0	51 s-a-0	52 s-a-1	53 s-a-1	54 s-a-1
55 s-a-1	56 s-a-0	58 s-a-0	64 s-a-1	66 s-a-0	67 s-a-1	68 s-a-1	95 s-a-0
102 s-a-0	103 s-a-0	104 s-a-0	107 s-a-1	108 s-a-1	109 s-a-1	110 s-a-1	111 s-a-1
113 s-a-1	115 s-a-1	116 s-a-1	118 s-a-0	119 s-a-0	121 s-a-0	122 s-a-0	132 s-a-0
133 s-a-0	135 s-a-0	138 s-a-0	143 s-a-1	144 s-a-1	145 s-a-1	149 s-a-0	152 s-a-0
158 s-a-0	159 s-a-0	161 s-a-0	163 s-a-0	166 s-a-1	167 s-a-1	168 s-a-1	169 s-a-1
170 s-a-1	173 s-a-0	182 s-a-1	183 s-a-1	186 s-a-1	187 s-a-1	188 s-a-1	

Circuit: s298f_2

- Input Vector: 1 1 1 0 1 1 1 0 1 0 1 1 1 0 1 1 1
- Detected Faults: 53

Table 6: s298f_2 (11101110101110111)

1 s-a-0	6 s-a-0	7 s-a-0	8 s-a-1	9 s-a-0	10 s-a-1	11 s-a-0	12 s-a-0	15 s-a-0
18 s-a-1	19 s-a-1	20 s-a-1	21 s-a-1	22 s-a-1	23 s-a-1	24 s-a-1	25 s-a-1	26 s-a-1
27 s-a-1	28 s-a-1	29 s-a-1	30 s-a-1	31 s-a-1	32 s-a-0	33 s-a-0	34 s-a-0	35 s-a-1
36 s-a-0	37 s-a-1	43 s-a-0	45 s-a-1	47 s-a-1	49 s-a-1	51 s-a-1	53 s-a-0	55 s-a-0
57 s-a-0	59 s-a-0	63 s-a-1	64 s-a-0	65 s-a-1	66 s-a-1	67 s-a-1	68 s-a-1	102 s-a-1
152 s-a-1	166 s-a-0	168 s-a-0	170 s-a-0	172 s-a-0	173 s-a-0	174 s-a-0	182 s-a-0	

Circuit: s344f_2

- Input Vector: 1 0 1 0 1 0 1 0 1 0 1 0 1 1 1 1 0 1 1 1 1 1 1
- Detected Faults: 82

Table 7: s344f_2 (101010101010111101111111)

1 s-a-0	2 s-a-1	3 s-a-0	4 s-a-1	5 s-a-0	6 s-a-1	7 s-a-0	8 s-a-1	9 s-a-0
10 s-a-1	11 s-a-0	12 s-a-1	13 s-a-0	14 s-a-0	15 s-a-0	16 s-a-0	25 s-a-1	26 s-a-1
27 s-a-1	28 s-a-0	29 s-a-0	30 s-a-0	31 s-a-0	32 s-a-1	33 s-a-0	34 s-a-1	35 s-a-0
36 s-a-1	37 s-a-0	38 s-a-0	39 s-a-0	40 s-a-1	41 s-a-0	42 s-a-1	43 s-a-0	44 s-a-1
45 s-a-0	46 s-a-1	47 s-a-0	48 s-a-0	49 s-a-1	50 s-a-0	54 s-a-1	60 s-a-0	61 s-a-1
62 s-a-1	64 s-a-0	65 s-a-1	66 s-a-1	67 s-a-0	68 s-a-1	69 s-a-1	70 s-a-1	71 s-a-1
72 s-a-1	73 s-a-1	76 s-a-1	77 s-a-1	78 s-a-1	91 s-a-0	92 s-a-1	95 s-a-1	96 s-a-1
97 s-a-0	99 s-a-0	101 s-a-0	105 s-a-1	106 s-a-0	108 s-a-0	109 s-a-1	110 s-a-1	111 s-a-1
112 s-a-0	114 s-a-0	115 s-a-1	116 s-a-1	144 s-a-0	145 s-a-0	146 s-a-0	188 s-a-1	189 s-a-1
190 s-a-1								

Circuit: s344f_2

- Input Vector: 1 1 1 0 1 0 1 1 1 0 1 0 1 0 1 0 0 0 1 1 0 0
- Detected Faults: 132

Table 8: s344f_2 (111010111010101010001100)

1 s-a-0	2 s-a-0	3 s-a-0	4 s-a-1	5 s-a-0	6 s-a-1	7 s-a-0	8 s-a-0	9 s-a-0
10 s-a-1	11 s-a-0	12 s-a-1	13 s-a-0	14 s-a-1	15 s-a-0	16 s-a-1	25 s-a-1	26 s-a-1
27 s-a-1	28 s-a-0	29 s-a-1	30 s-a-0	31 s-a-1	32 s-a-0	33 s-a-0	34 s-a-0	35 s-a-1
36 s-a-1	37 s-a-0	38 s-a-1	39 s-a-0	40 s-a-1	41 s-a-0	42 s-a-1	43 s-a-0	44 s-a-1
45 s-a-0	46 s-a-1	47 s-a-1	48 s-a-1	49 s-a-0	50 s-a-1	51 s-a-0	52 s-a-0	53 s-a-1
55 s-a-0	56 s-a-1	57 s-a-0	58 s-a-1	59 s-a-1	60 s-a-1	61 s-a-1	62 s-a-1	63 s-a-1
64 s-a-1	65 s-a-0	67 s-a-0	68 s-a-1	69 s-a-0	70 s-a-1	71 s-a-0	72 s-a-0	73 s-a-1
76 s-a-0	78 s-a-0	79 s-a-0	80 s-a-0	82 s-a-0	85 s-a-0	86 s-a-0	88 s-a-0	91 s-a-1
92 s-a-0	93 s-a-0	94 s-a-0	95 s-a-1	96 s-a-1	97 s-a-0	99 s-a-1	100 s-a-1	101 s-a-0
103 s-a-0	104 s-a-1	117 s-a-0	118 s-a-1	119 s-a-1	120 s-a-1	122 s-a-0	123 s-a-0	124 s-a-1
125 s-a-1	126 s-a-0	127 s-a-1	128 s-a-1	130 s-a-0	131 s-a-0	132 s-a-1	133 s-a-1	134 s-a-1
136 s-a-0	137 s-a-1	138 s-a-1	139 s-a-1	140 s-a-1	142 s-a-0	144 s-a-0	146 s-a-0	147 s-a-1
148 s-a-1	149 s-a-0	153 s-a-1	154 s-a-1	155 s-a-0	156 s-a-0	162 s-a-1	163 s-a-1	164 s-a-1
165 s-a-0	169 s-a-1	170 s-a-0	171 s-a-0	173 s-a-1	174 s-a-1	175 s-a-0	179 s-a-0	181 s-a-1
182 s-a-1	183 s-a-1	184 s-a-1	186 s-a-1	188 s-a-0	189 s-a-0			

Circuit: s349f_2

- Input Vector: 1 0 1 0 0 0 0 0 0 1 0 1 0 1 1 1 1 1 1 1 1
- Detected Faults: 97

Table 9: s349f_2 (10100000001010101111111)

1 s-a-0	2 s-a-1	3 s-a-0	4 s-a-1	5 s-a-1	6 s-a-1	7 s-a-1	8 s-a-1	9 s-a-1
10 s-a-1	11 s-a-0	12 s-a-1	13 s-a-0	14 s-a-1	15 s-a-0	16 s-a-1	25 s-a-0	26 s-a-1
27 s-a-0	28 s-a-1	29 s-a-1	30 s-a-1	31 s-a-1	32 s-a-1	33 s-a-1	34 s-a-1	35 s-a-0
36 s-a-1	37 s-a-0	38 s-a-1	39 s-a-0	40 s-a-1	41 s-a-0	42 s-a-0	43 s-a-1	44 s-a-0
45 s-a-0	46 s-a-0	47 s-a-0	48 s-a-0	49 s-a-0	50 s-a-0	51 s-a-1	52 s-a-0	53 s-a-1
54 s-a-1	55 s-a-1	56 s-a-1	57 s-a-1	58 s-a-0	60 s-a-0	62 s-a-0	64 s-a-1	65 s-a-1
66 s-a-0	67 s-a-1	68 s-a-0	69 s-a-1	70 s-a-1	71 s-a-1	72 s-a-1	73 s-a-1	74 s-a-1
109 s-a-0	111 s-a-0	113 s-a-0	115 s-a-0	116 s-a-1	118 s-a-1	120 s-a-0	121 s-a-1	123 s-a-0
124 s-a-1	126 s-a-0	127 s-a-0	128 s-a-1	129 s-a-1	130 s-a-1	131 s-a-1	133 s-a-0	134 s-a-1
135 s-a-1	137 s-a-0	138 s-a-1	171 s-a-0	173 s-a-0	174 s-a-1	176 s-a-0	177 s-a-1	178 s-a-1
179 s-a-0	180 s-a-0	181 s-a-0	183 s-a-0	187 s-a-1	188 s-a-1	189 s-a-1		

Circuit: s349f_2

- Input Vector: 1 1 1 1 1 1 1 0 1 0 1 0 1 0 1 0 0 0 1 1 1 1
- Detected Faults: 137

Table 10: s349f_2 (111111101010101010001111)

1 s-a-0	2 s-a-0	3 s-a-0	4 s-a-0	5 s-a-0	6 s-a-0	7 s-a-0	8 s-a-1	9 s-a-0
10 s-a-1	11 s-a-0	12 s-a-1	13 s-a-0	14 s-a-1	15 s-a-0	25 s-a-1	26 s-a-1	27 s-a-1
28 s-a-0	29 s-a-0	30 s-a-0	31 s-a-0	32 s-a-0	33 s-a-1	34 s-a-0	35 s-a-1	36 s-a-1
37 s-a-0	38 s-a-1	39 s-a-0	40 s-a-0	41 s-a-1	42 s-a-1	43 s-a-1	44 s-a-0	45 s-a-1
46 s-a-0	47 s-a-1	48 s-a-1	49 s-a-1	50 s-a-1	51 s-a-0	52 s-a-0	53 s-a-0	54 s-a-0
55 s-a-0	56 s-a-0	57 s-a-0	58 s-a-1	59 s-a-1	61 s-a-0	62 s-a-1	63 s-a-1	65 s-a-0
66 s-a-0	67 s-a-1	68 s-a-0	69 s-a-1	70 s-a-0	71 s-a-0	72 s-a-0	74 s-a-0	75 s-a-0
76 s-a-1	77 s-a-1	78 s-a-0	79 s-a-1	80 s-a-1	81 s-a-0	82 s-a-1	83 s-a-1	84 s-a-0
85 s-a-1	86 s-a-1	87 s-a-0	88 s-a-1	89 s-a-1	90 s-a-0	91 s-a-1	92 s-a-1	93 s-a-0
94 s-a-0	95 s-a-0	96 s-a-1	97 s-a-0	99 s-a-0	102 s-a-0	103 s-a-0	105 s-a-0	108 s-a-1
109 s-a-1	110 s-a-1	111 s-a-1	112 s-a-1	113 s-a-1	114 s-a-1	115 s-a-1	116 s-a-0	117 s-a-0
130 s-a-1	131 s-a-1	133 s-a-0	134 s-a-1	135 s-a-1	137 s-a-0	138 s-a-1	143 s-a-1	144 s-a-1
145 s-a-1	150 s-a-1	151 s-a-1	152 s-a-1	157 s-a-1	158 s-a-1	159 s-a-1	162 s-a-1	163 s-a-1
164 s-a-1	165 s-a-1	166 s-a-1	167 s-a-0	168 s-a-1	169 s-a-0	171 s-a-0	173 s-a-0	174 s-a-0
175 s-a-0	177 s-a-0	180 s-a-1	181 s-a-1	182 s-a-1	183 s-a-1	184 s-a-1	185 s-a-1	186 s-a-1
187 s-a-0	188 s-a-0							